

Boolean Algebra

Summer 21

Asst. Prof. Nattapol Aunsri, Ph.D.
IATE Research Unit
CCC Research Group
School of Information Technology, MFU

**Prepared for Digital Industry Integration: DII,
CAMT, CMU**

Outline

- ▶ Boolean Algebra
 - Basic Boolean Equations
 - Multiple Level Logic Representation
 - Basic Identities
 - Algebraic Manipulation
 - Complements and Duals

Basic Boolean Equations

Basic gates/functions

▶ AND

- $Z = A B$

- $X = C D E$

3 input gate

- $Y = F G H K$

4 input gate

▶ OR

- $Z = A + B$

- $Y = F + G + H + K$

4 input gate

▶ NOT

- $Z = \bar{A}$

- $Y = \overline{(F G H K)}$

actually 2 level logic

Level Logic





- ▶ Consider the following logic equation
 - $Z(A,B,C,D) = A B + C D$
 - The $Z(A,B,C,D)$ means that the output is a function of the four variables within the ().
 - The AB and CD are terms of the expression.
 - This form of representing the function is an algebraic expression.
 - For this function to be True, either both A AND B are True OR both C AND D are True.

Logic Gates

- ▶ Inverter, Or, And, XOR gate symbols, etc.
- ▶ Multi-input gates.
- ▶ Logic circuits and examples.
- ▶ Adders, “half,” “full,” and n -bit.


Logic Gate Symbols

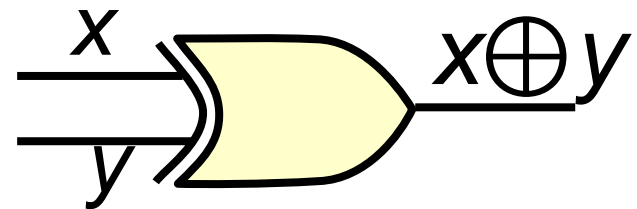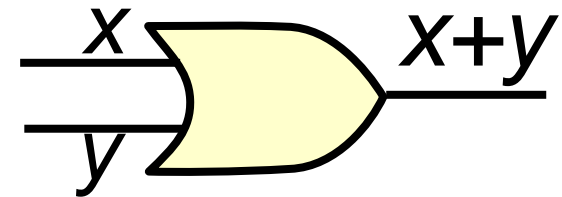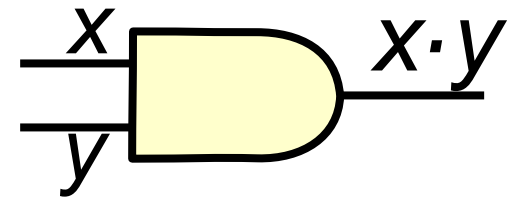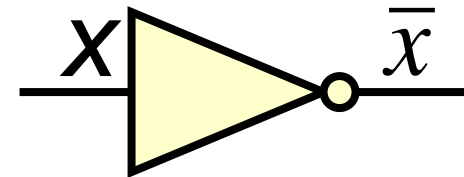- ▶ Inverter (logical NOT, Boolean complement).
- ▶ AND gate (Boolean product).
- ▶ OR gate (Boolean sum).
- ▶ XOR gate (exclusive-OR, sum mod 2).






Multi-input

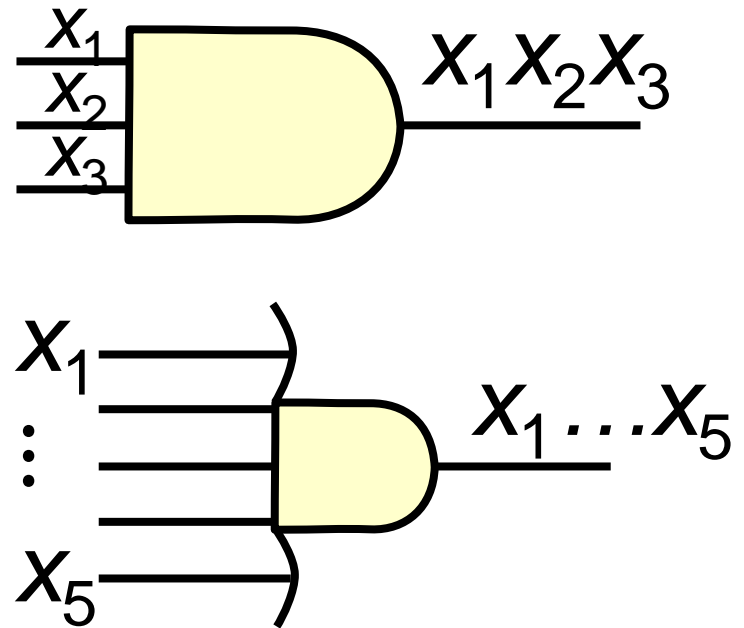- ▶ Can extend these gates to arbitrarily many inputs.
- ▶ Two commonly seen drawing styles:
 - Note that the second style keeps the gate icon relatively small.




NAND, NOR, XNOR

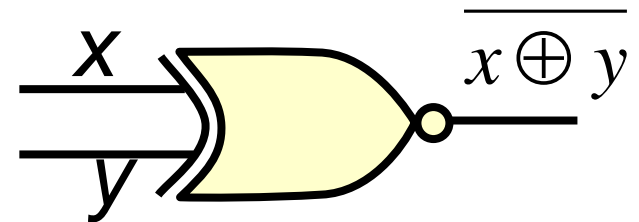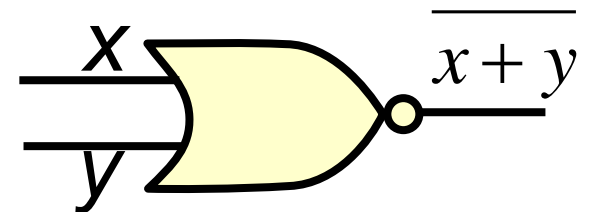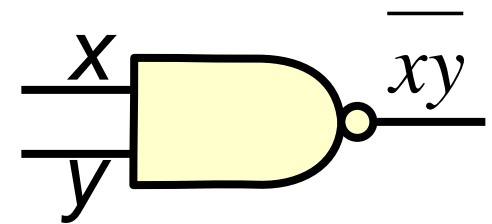- ▶ Just like the earlier icons, but with a small circle on the gate's output.
 - Denotes that output is complemented.
- ▶ The circles can also be placed on inputs.
 - Means, input is complemented before being used.




Buffer

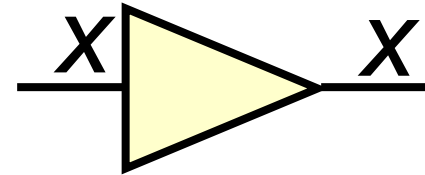- ▶ What about an inverter symbol *without* a circle?
- ▶ This is called a *buffer*.
- ▶ It is the identity function.



Logic Gates

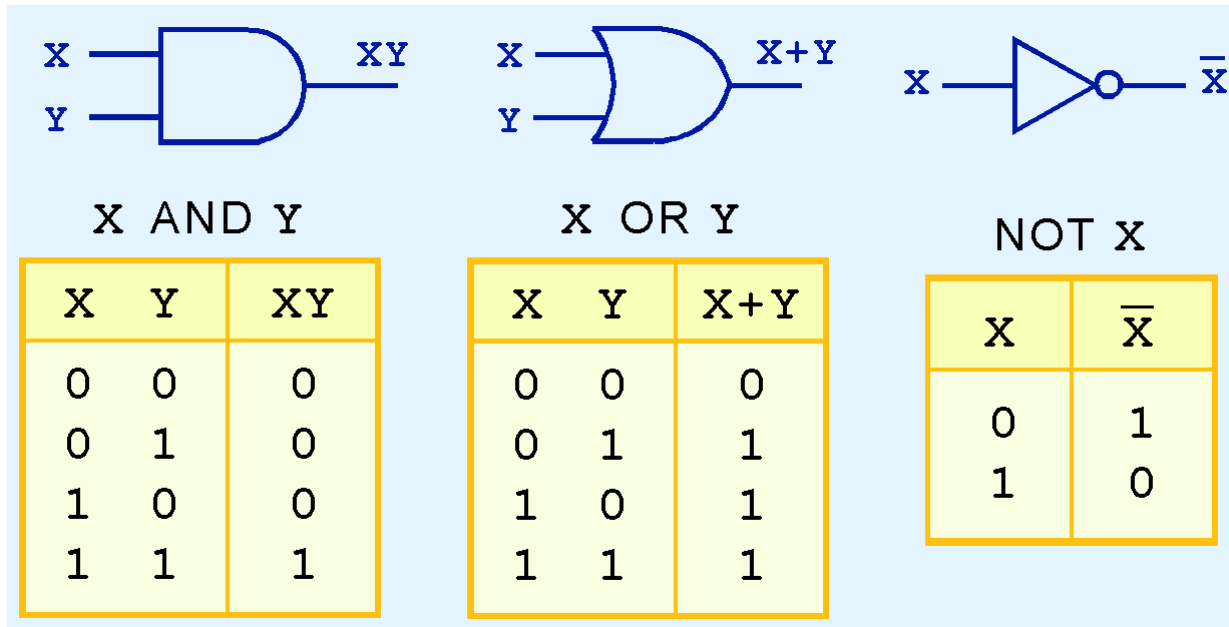- The three simplest gates are the AND, OR, and NOT gates.




- They correspond directly to their respective Boolean operations, as you can see by their truth tables.
- And these representations map exactly into the transistors on the last two slides.

Logic Gates

X XOR Y

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0


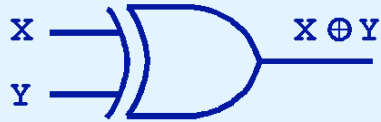


- The output of the XOR operation is true only when the values of the inputs differ.

Note the special symbol \oplus for the XOR operation.

X NAND Y

X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

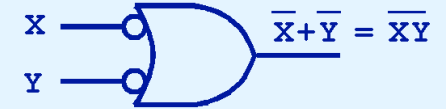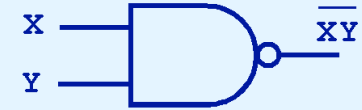


X NOR Y

X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0





- Symbols for NAND and NOR, and truth tables are shown at the right.

Logic Gates

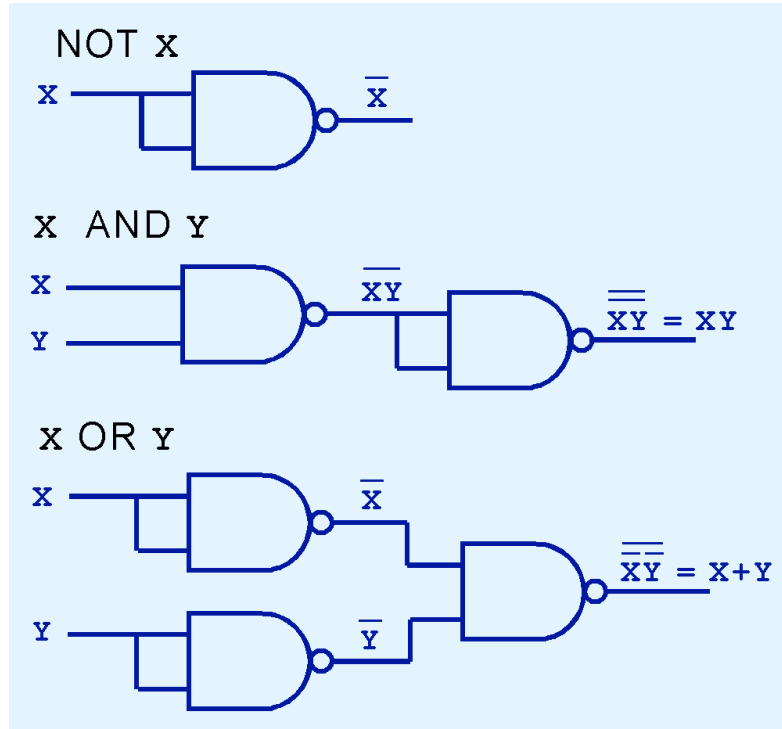

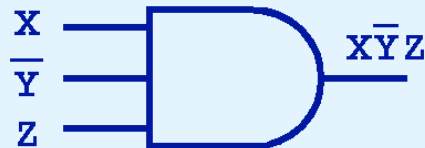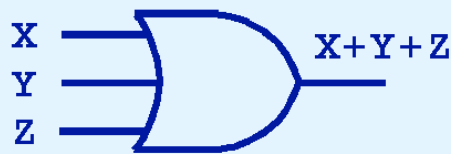
- NAND and NOR are known as *universal gates* because they are inexpensive to manufacture and any Boolean function can be constructed using only NAND or only NOR gates.
- Gates can have multiple inputs and more than one output. A second output can be provided for the complement of the operation. We'll see more of this later.



Digital Components

- Combinations of gates implement Boolean functions.
- The circuit below implements the function:


$$F(X, Y, Z) = X + \bar{Y}Z$$

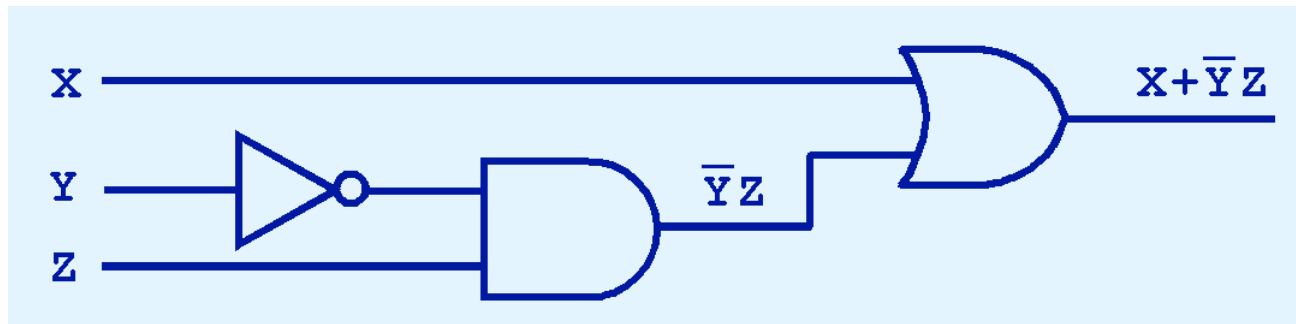

- This is an example of a *combinational logic* circuit.
- Combinational logic circuits produce a specified output (almost) at the instant when input values are applied. Later we'll explore circuits where this is not the case.

Truth table expression

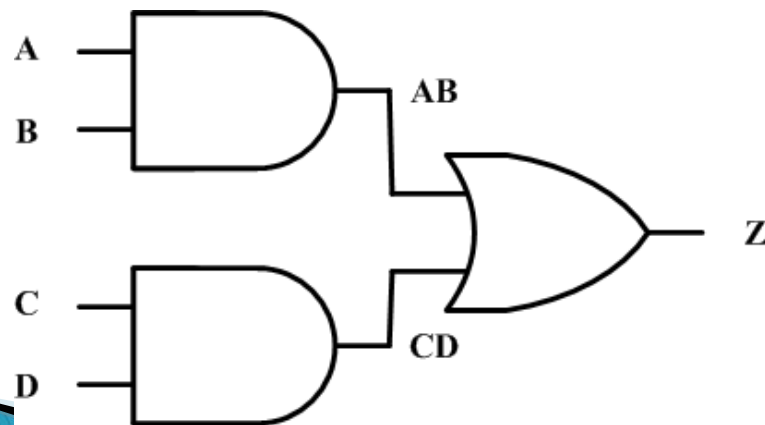- Just like we had the truth tables for the basic functions, we can also construct truth tables for any function.



A	B	C	D	Z	AB	CD
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	1	0	1
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	0	0
0	1	1	1	1	0	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	0
1	1	1	1	1	1	1

Examples of Boolean Equations

► Some examples

- $F = AB + CD + BD'$
- $Y = CD + A'B'$
- $SUM = AB + AC + BC$
- $P = A_0A_1A_2A_3A_4B_0B_1B_2B_3B_4 + \dots$
- Equations can be very complex
- Usually desire a minimal expression

Basic Identities of Boolean Algebra

▶ 1. $X + 0 = X$

OR +

A	0	RESULT
0	0	0
1	0	1

▶ 3. $X + 1 = 1$

▶ 5. $X + X = X$

▶ 2. $X \cdot 1 = X$

AND •

A	1	RESULT
0	1	0
1	1	1

▶ 4. $X \cdot 0 = 0$

▶ 6. $X \cdot X = X$

Basic Identities (2)

▶ 7. $X + X' = 1$

X	X'	RES
0	1	1
1	0	1

▶ 8. $X \cdot X' = 0$

X	X'	RES
0	1	0
1	0	0

▶ 9. $(X')' = X$

Basic Properties (Laws)

▶ Commutative

- 10. $X + Y = Y + X$

▶ Associative

- 12. $X + (Y + Z) = (X + Y) + Z$

▶ Distributive

- 14. $X(Y + Z) = XY + XZ$
- AND distributes over OR

▶ Commutative

- 11. $X \cdot Y = Y \cdot X$

▶ Associative

- 13. $X(YZ) = (XY)Z$

▶ Distributive

- 15. $X + YZ = (X + Y)(X + Z)$
- OR distributes over AND

Basic Properties (2)

- ▶ DeMorgan's Theorem
- ▶ Very important in simplifying equations
 - 16. $(X + Y)' = X' \cdot Y'$
 - 17. $(XY)' = X' + Y'$

X	Y	X+Y	$\overline{X+Y}$	X	Y	\overline{X}	\overline{Y}	$\overline{X} \cdot \overline{Y}$
0	0	0	1	0	0	1	1	1
0	1	1	0	0	1	1	0	0
1	0	1	0	1	0	0	1	0
1	1	1	0	1	1	0	0	0

Simplification

- ▶ These properties (Laws and Theorems) can be used to simplify equations to their simplest form.
 - Simplify $F = X'YZ + X'Y\bar{Z} + XZ$

$$F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$$


$$= \bar{X}Y(Z + \bar{Z}) + XZ \quad \text{by identity 14}$$

$$= \bar{X}Y \cdot 1 + XZ \quad \text{by identity 7}$$


$$= \bar{X}Y + XZ \quad \text{by identity 2}$$

Affect on implementation

► $F = X'YZ + X'YZ' + XZ$

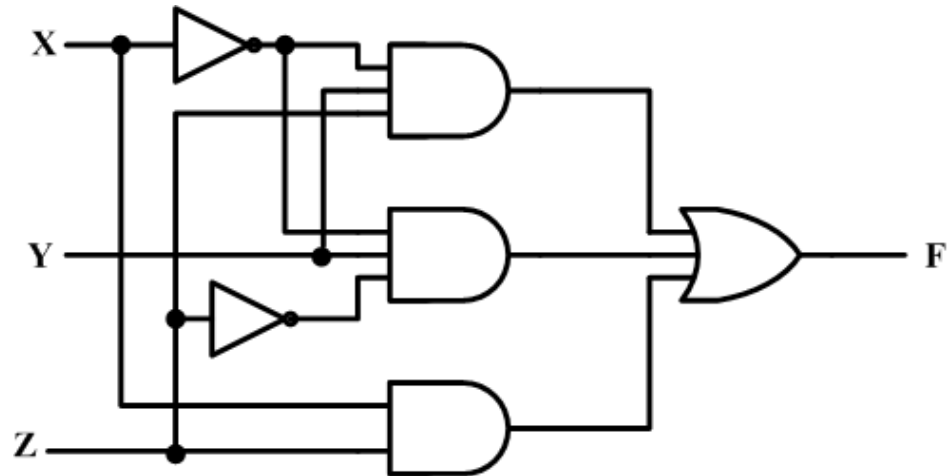

► Reduces to $F = X'Y + XZ$

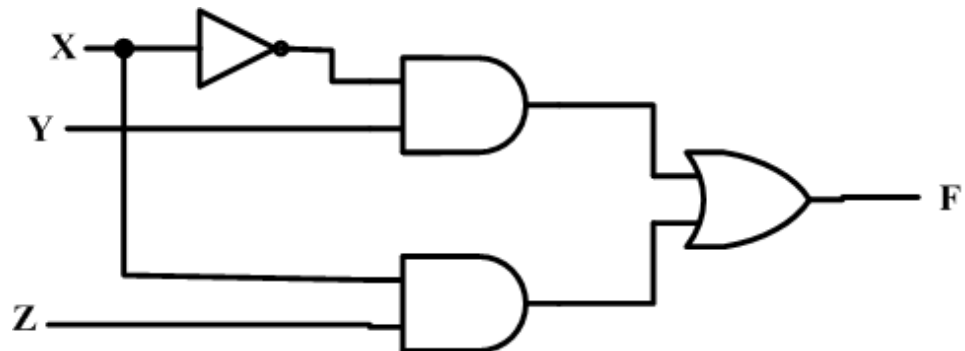

More examples

► Examples of simplification

◦ 1. $X + XY = X \cdot 1 + XY = X(1 + Y) = X \cdot 1 = X$

• Use $\begin{matrix} 2 & 14 & 3 & 2 \end{matrix}$

◦ 2. $XY + XY' = X(Y + Y') = X \cdot 1 = X$

• Use $\begin{matrix} 14 & 7 & 2 \end{matrix}$

◦ 3. $X + X'Y = (X + X')(X + Y) = 1 \cdot (X + Y) = X + Y$

• Use $\begin{matrix} 15 & 7 & 2 \end{matrix}$

Further Examples

► Examples from the text

- 4. $X \cdot (X+Y) = X \cdot X + X \cdot Y = X + XY = X(1+Y) = X \cdot 1 = X$
 - Use $\begin{matrix} 1 & 4 & 6 & 1 & 4 & 3 & 2 \end{matrix}$
- 5. $(X+Y) \cdot (X+Y') = XX + XY' + XY + YY' =$
- $X + XY' + XY + 0 = X(1 + Y' + Y) = X \cdot 1 = X$
- by a slightly different reduction
- 6. $X(X' + Y) = XX' + XY = 0 + XY = XY$

Consensus Theorem

- ▶ The Consensus Theorem states that

$$XY + X'Z + YZ = XY + X'Z$$

- ▶ This can be considered as **redundancy trick**.

Application of Consensus Theorem

- ▶ Consider

- $(A+B)(A'+C) = AA' + AC + A'B + BC$
 $= AC + A'B + BC$
 $= AC + A'B$

- ▶ Use consensus theorem to simplify the followings:

- $AB' + BC + AC$
 - $(A+B)(A'+C)(B+C)$
 - $A'B' + B'C' + AC'$

Application of Consensus Theorem

- ▶ Consider

- $(A+B)(A'+C) = AA' + AC + A'B + BC$
 $= AC + A'B + BC$
 $= AC + A'B$

- ▶ Use consensus theorem to simplify the followings:

- $AB' + BC + AC = AB' + BC$
 - $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$
 - $A'B' + B'C' + AC' = A'B' + AC'$

Complement of a function

- ▶ In real implementation sometimes the complement of a function is needed.
 - Have $F = X'YZ' + X'Y'Z$

$$F = \overline{X}Y\overline{Z} + \overline{X}\overline{Y}Z$$

$$\overline{F} = \overline{\overline{X}Y\overline{Z} + \overline{X}\overline{Y}Z}$$

$$= (\overline{\overline{X}Y\overline{Z}}) \cdot (\overline{\overline{X}\overline{Y}Z})$$

$$= (X + \overline{Y} + Z) \cdot (X + Y + \overline{Z})$$

Duals

- ▶ What is meant by the dual of a function?
 - The *dual* of a function is obtained by interchanging OR and AND operations and replacing 1s and 0s with 0s and 1s.
- ▶ Shortcut to getting function complement
 - Starting with the equation on the previous slide
 - Generate the dual $F = (X' + Y + Z')(X' + Y' + Z)$
 - Complement each literal to get:
 - $F' = (XY'Z) + (XYZ')$

Thanks

Q & A